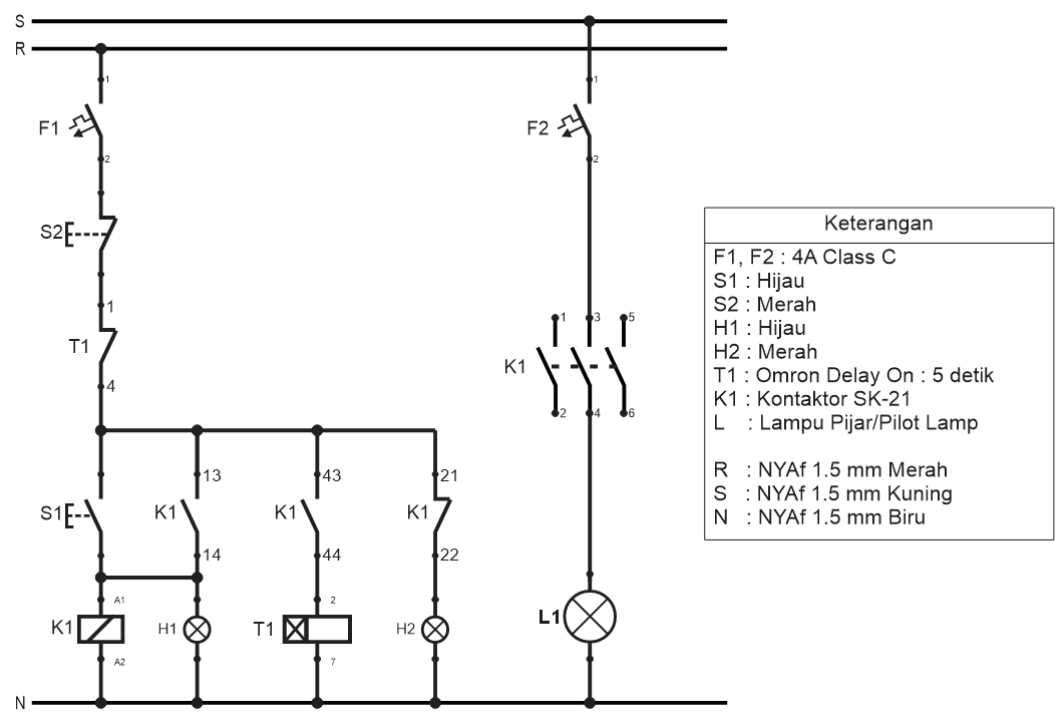


JOB ORDER 4		
KENDALI MOTOR MATI OTOMATIS		
Nama :	Tanggal :	Diisi Guru :
		Selesai Praktek :
Kelas :	Mulai :	Selesai Laporan :

A. KOMPETENSI

1. Merangkai Timer Omron pada rangkaian kendali motor

B. GAMBAR RANGKAIAN



C. KEBUTUHAN BAHAN

No	Nama	Jumlah

D. CARA KERJA RANGKAIAN

.....

.....

.....

.....

.....

.....




.....

F. FUNGSI KOMPONEN

Komponen	Fungsi
F1, F2	
S1	
S2	
K1	
T1	
H1	
H2	

G. HASIL PENGUJIAN

No	Aksi	Reaksi	Tegangan
1	S1		
	• S1 ditekan		K1 : H1 :
	• S1 dilepas		H2 : L1 :
2	S2		
	• S2 ditekan		K1 : H1 :
	• S2 dilepas		H2 : L1 :

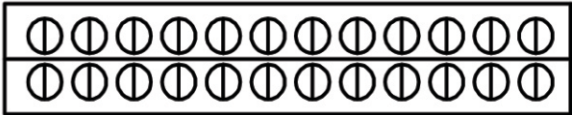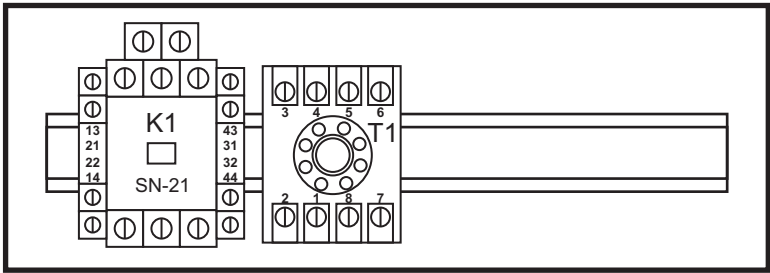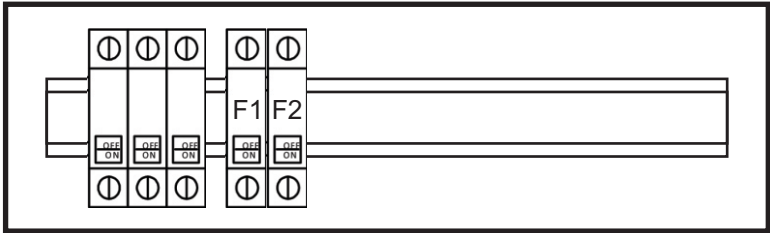

Keterangan

F1,F2 :
K1 :
T1 :
H1 :
H2 :
S1 :
S2 :
L1 :

GAMBAR PELAKSANAAN
KENDALI MOTOR MATI OTOMATIS

SMK NEGERI 3 YOGYAKARTA

GB 01/JOB 4/F4

Skala

Digambar

1 : 1

Diperiksa

NUR FAUZI

Tanggal

Kelas/Absen