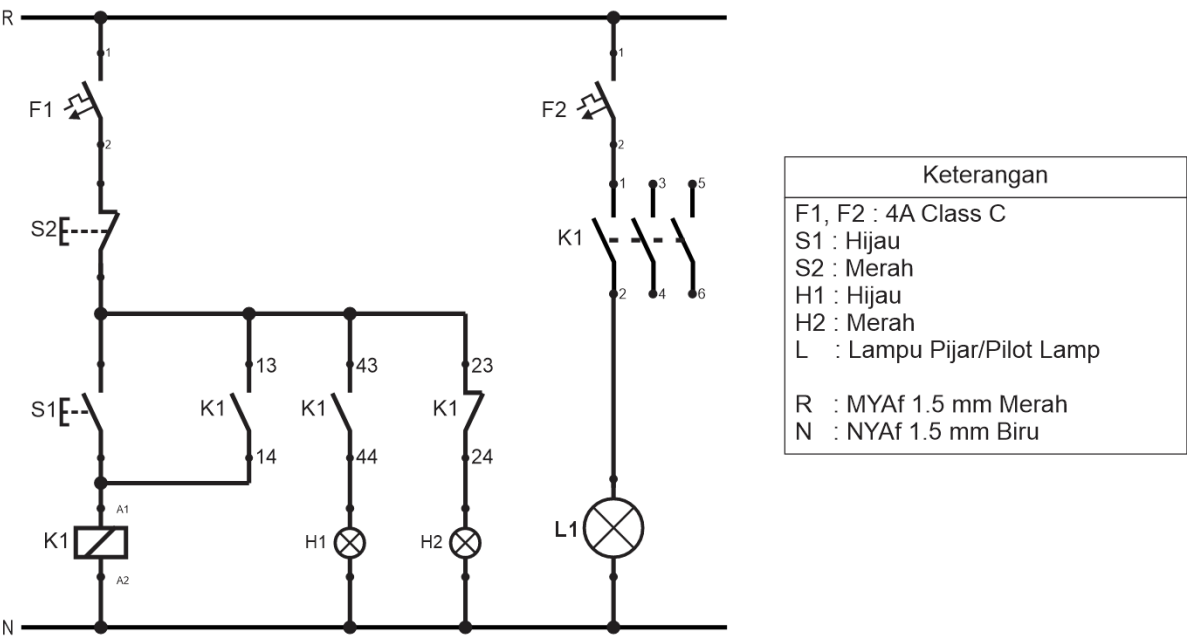


JOB ORDER 3		
SISTEM MINIMUM KENDALI DIRECT ON LINE (DOL)		
Nama :	Tanggal :	Selesai :
Kelas :	Mulai :	Paraf Guru :

A. KOMPETENSI

1. Merangkai sistem minimum pengendalian DOL

B. GAMBAR RANGKAIAN



C. KEBUTUHAN BAHAN

No	Nama	Jumlah

D. CARA KERJA RANGKAIAN

.....

.....

.....

.....

.....




.....

F. FUNGSI KOMPONEN

Komponen	Fungsi
F1	
F2	
S1	
S2	
K1	
H1	
H2	

G. HASIL PENGUJIAN

No	Aksi	Reaksi	Tegangan
1	S1		
	• S1 ditekan		K1 : H1 : H2 : L1 :
	• S1 dilepas		
2	S2		
	• S2 ditekan		K1 : H1 : H2 : L1 :
	• S2 dilepas		

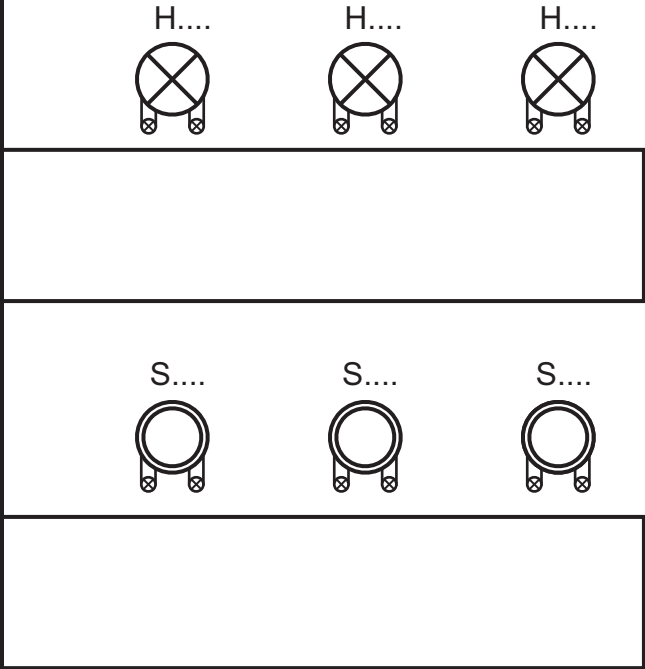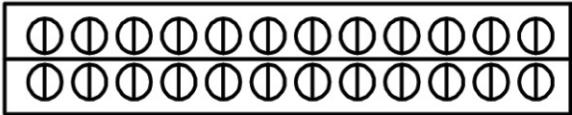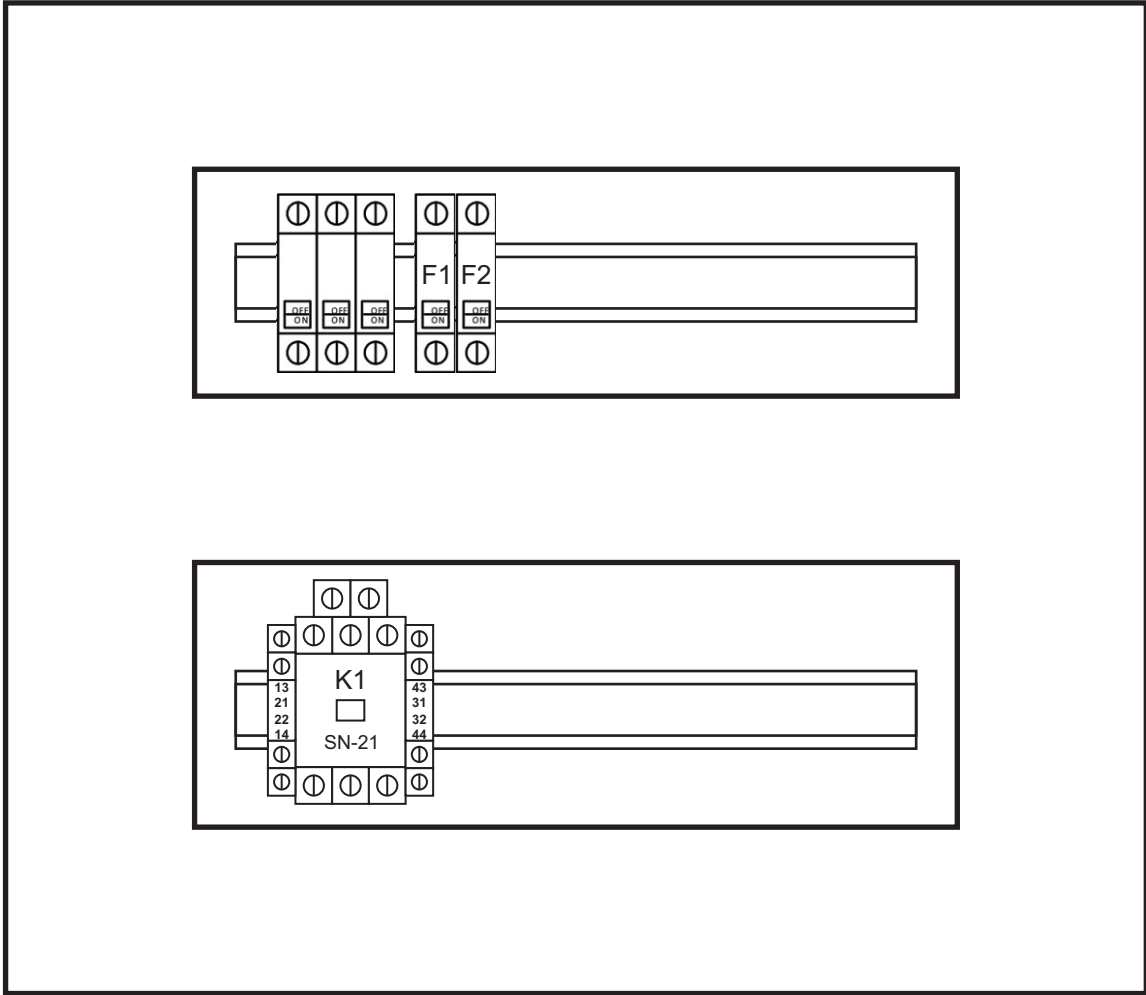

Keterangan	
F1,F2 :	
K1 :	
H1 :	
H2 :	
S1 :	
S2 :	
L1 :	

GAMBAR PELAKSANAAN
SISTEM MINIMUM KENDALI DOL

1 : 1	Skala	Digambar		
		Diperiksa	NUR FAUZI	
		Tanggal		
		Kelas/Absen		